

ECE 476 – Power System Analysis Fall 2017

Homework 6

Reading: Chapter 6 of textbook

In-class quiz: Tuesday October 17, 2017

Problem 1. Compute the elements of the **third** row of Y_{bus} for the power system in Example 6.9 of textbook.

Solution. We find each entry in the third row of the admittance matrix as follows:

$$\bar{Y}_{31} = \bar{Y}_{32} = \bar{Y}_{35} = 0.$$

$$\bar{Y}_{34} = \frac{-1}{R_{34} + jX_{34}} = \frac{-1}{0.00075 + j0.01} = -7.458 + j99.44 \text{ p.u.}$$

$$\bar{Y}_{33} = \frac{1}{R_{34} + jX_{34}} + j\frac{B'_{34}}{2} = \frac{1}{0.00075 + j0.01} + j\frac{0}{2} = 7.458 - j99.44 \text{ p.u.}$$

So the third row of the admittance matrix is

$$\bar{Y}_3 = [0 \quad 0 \quad 7.458 - j99.44 \quad -7.458 + j99.44 \quad 0].$$

Problem 2. Given the impedance diagram of a simple system as shown in Figure 1, draw the admittance diagram for the system and develop the 4 x 4 bus admittance matrix Y_{bus} by inspection.

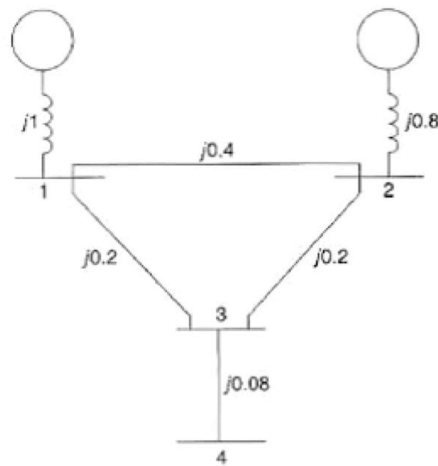


Figure 1: System diagram for problem 2.

Solution. The admittance diagram is shown in Figure 2.

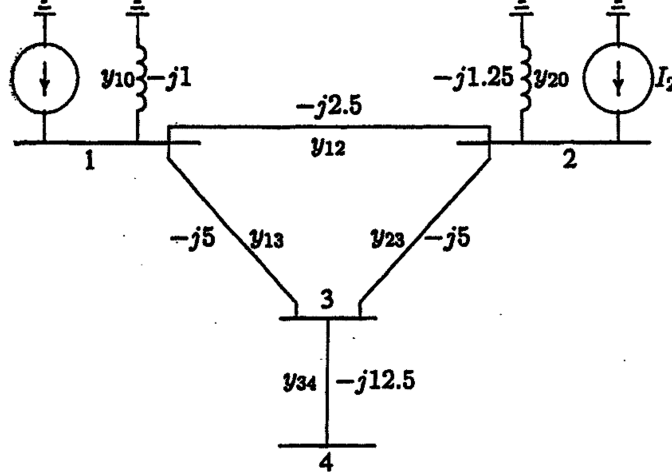


Figure 2: Admittance diagram for Problem 2

The structure of the admittance matrix is given as

$$\bar{Y}_{\text{bus}} = \begin{bmatrix} \bar{Y}_{11} & \bar{Y}_{12} & \bar{Y}_{13} & \bar{Y}_{14} \\ \bar{Y}_{21} & \bar{Y}_{22} & \bar{Y}_{23} & \bar{Y}_{24} \\ \bar{Y}_{31} & \bar{Y}_{32} & \bar{Y}_{33} & \bar{Y}_{34} \\ \bar{Y}_{41} & \bar{Y}_{42} & \bar{Y}_{43} & \bar{Y}_{44} \end{bmatrix},$$

where the components are found as follows

$$\begin{aligned} \bar{Y}_{11} &= \bar{y}_{10} + \bar{y}_{12} + \bar{y}_{13} & \bar{Y}_{22} &= \bar{y}_{20} + \bar{y}_{12} + \bar{y}_{23} \\ \bar{Y}_{23} &= \bar{y}_{13} + \bar{y}_{23} + \bar{y}_{34} & \bar{Y}_{44} &= \bar{y}_{34} \\ \bar{Y}_{12} &= \bar{Y}_{21} = -\bar{y}_{12} & \bar{Y}_{13} &= \bar{Y}_{31} = -\bar{y}_{13} \\ \bar{Y}_{23} &= \bar{Y}_{32} = -\bar{y}_{23} & \bar{Y}_{34} &= \bar{Y}_{43} = -\bar{y}_{34}. \end{aligned}$$

Plugging in the values from the admittance diagram, the admittance matrix becomes

$$\bar{Y}_{\text{bus}} = j \begin{bmatrix} -8.5 & 2.5 & 5.0 & 0 \\ 2.5 & -8.75 & 5.0 & 0 \\ 5.0 & 5.0 & -22.5 & 12.5 \\ 0 & 0 & 12.5 & -12.5 \end{bmatrix} \text{ S.}$$

Problem 3. A load L consuming 1 p.u. of active power and 0.5 p.u. of reactive power is connected to a generator $G1$ through a short transmission line with $Z' = 0.02 + j0.06$ p.u. Also, there is a capacitor connected to the load bus with admittance $Y_{\text{cap}} = j0.25$ p.u. The generator voltage is voltage $V_{G1} = 1 \angle 0^\circ$.

Solution

- The one line diagram is shown in Figure 3.
- The admittance matrix can be found by inspection as

$$\bar{Y} = \begin{bmatrix} 5 - j15 & -5 + j15 \\ -5 + j15 & 5 - j14.75 \end{bmatrix}.$$

- The power flow equations can now be written for each bus.
Bus 1:

$$\begin{aligned} P_1 &= V_1^2 G_{11} + V_1 V_2 [G_{12} \cos(\theta_1 - \theta_2) + B_{12} \sin(\theta_1 - \theta_2)] = 5 + V_2 [-5 \cos(\theta_2) - 15 \sin(\theta_2)] \\ Q_1 &= -V_1^2 B_{11} + V_1 V_2 [G_{12} \sin(\theta_1 - \theta_2) - B_{12} \cos(\theta_1 - \theta_2)] = 15 + V_2 [5 \sin(\theta_2) - 15 \cos(\theta_2)] \end{aligned}$$

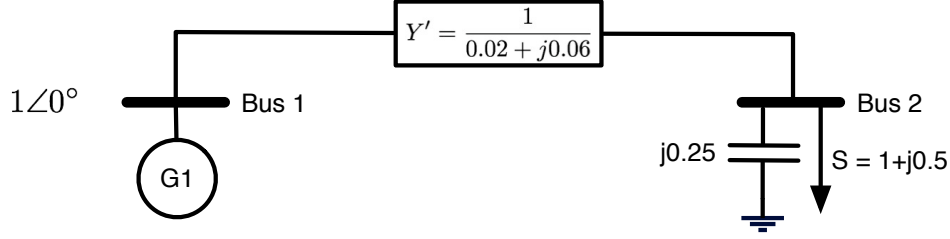


Figure 3: One Line Diagram

Bus 2:

$$P_2 = V_2^2 G_{22} + V_2 V_1 [G_{21} \cos(\theta_2 - \theta_1) + B_{21} \sin(\theta_2 - \theta_1)] = 5V_2^2 + V_2[-5 \cos(\theta_2) + 15 \sin(\theta_2)] = -1$$

$$Q_2 = -V_2^2 B_{22} + V_2 V_1 [G_{21} \sin(\theta_2 - \theta_1) - B_{21} \cos(\theta_2 - \theta_1)] = 14.75V_2^2 + V_2[-5 \sin(\theta_2) - 15 \cos(\theta_2)] = -0.5$$

Problem 4. Solve the following equation by the Newton-Raphson method:

$$2x_1^2 + x_2^2 - 8 = 0$$

$$x_1^2 - x_2^2 + x_1 x_2 - 4 = 0$$

Start with an initial guess of $x_1 = 1$ and $x_2 = 1$.

Solution. Define $\mathbf{x} = [x_1, x_2]^T$, and

$$\mathbf{f} = \begin{bmatrix} 2x_1^2 + x_2^2 - 8 \\ x_1^2 - x_2^2 + x_1 x_2 - 4 = 0 \end{bmatrix}.$$

Then,

$$\frac{\partial \mathbf{f}}{\partial \mathbf{x}} = \begin{bmatrix} 4x_1 & 2x_2 \\ 2x_1 + x_2 & -2x_2 + x_1 \end{bmatrix}.$$

The update rule using Newton-Raphson method is:

$$\mathbf{x}^{(k+1)} = \mathbf{x}^{(k)} - \left(\frac{\partial \mathbf{f}(\mathbf{x}^{(k)})}{\partial \mathbf{x}} \right)^{-1} \mathbf{f}(\mathbf{x}^{(k)})$$

After 4 iterations, you will get the solution $\mathbf{x} = [1.8091, 1.2060]^T$.

Problem 5. Assume a $1 + j0.5$ per unit load at bus 2 is being supplied by a generator at bus 1 through a transmission line with series impedance of $0.05 + j0.1$ per unit. Assuming bus 1 is the swing bus with a fixed per unit voltage of $1.0\angle 0^\circ$, use Newton-Raphson method to calculate the voltage at bus 2 after three iterations.

Solution. Similar to Problem 3, the admittance matrix can be found by inspection as

$$\bar{\mathbf{Y}} = \begin{bmatrix} 4 - j8 & -4 + j8 \\ -4 + j8 & 4 - j8 \end{bmatrix}.$$

The power flow equations at bus 2 are

$$P_2 = V_2^2 G_{22} + V_2 V_1 [G_{21} \cos(\theta_2 - \theta_1) + B_{21} \sin(\theta_2 - \theta_1)] = 4V_2^2 + V_2[-4 \cos(\theta_2) + 8 \sin(\theta_2)] = -1$$

$$Q_2 = -V_2^2 B_{22} + V_2 V_1 [G_{21} \sin(\theta_2 - \theta_1) - B_{21} \cos(\theta_2 - \theta_1)] = 8V_2^2 + V_2[-4 \sin(\theta_2) - 8 \cos(\theta_2)] = -0.5$$

Define $\mathbf{x} = [\theta_2, V_2]^\top$, and

$$\mathbf{f} = \begin{bmatrix} 4V_2^2 - 4V_2 \cos \theta_2 + 8V_2 \sin \theta_2 + 1 \\ 8V_2^2 - 4V_2 \sin \theta_2 - 8V_2 \cos \theta_2 + 0.5 \end{bmatrix}.$$

Then,

$$\frac{\partial \mathbf{f}}{\partial \mathbf{x}} = \begin{bmatrix} 4V_2 \sin \theta_2 + 8V_2 \cos \theta_2 & 8V_2 - 4 \cos \theta_2 + 8 \sin \theta_2 \\ -4V_2 \cos \theta_2 + 8V_2 \sin \theta_2 & 16V_2 - 4 \sin \theta_2 - 8 \cos \theta_2 \end{bmatrix}.$$

The update rule using Newton-Raphson method is:

$$\mathbf{x}^{(k+1)} = \mathbf{x}^{(k)} - \left(\frac{\partial \mathbf{f}(\mathbf{x}^{(k)})}{\partial \mathbf{x}} \right)^{-1} \mathbf{f}(\mathbf{x}^{(k)})$$

The iteration process is shown below:

$$\begin{aligned} \mathbf{x}^{(0)} &= [0, 1]^\top \\ \mathbf{f}(\mathbf{x}^{(0)}) &= [1.0, 0.5]^\top \\ \frac{\partial \mathbf{f}(\mathbf{x}^{(0)})}{\partial \mathbf{x}} &= \begin{bmatrix} 8 & 4 \\ 0 & 8 \end{bmatrix} \end{aligned}$$

$$\begin{aligned} \mathbf{x}^{(1)} &= [-0.0938, 0.9375]^\top \\ \mathbf{f}(\mathbf{x}^{(1)}) &= [0.0800, 0.4152]^\top \\ \frac{\partial \mathbf{f}(\mathbf{x}^{(1)})}{\partial \mathbf{x}} &= \begin{bmatrix} 7.1160 & 2.7687 \\ -0.3510 & 7.4096 \end{bmatrix} \end{aligned}$$

$$\begin{aligned} \mathbf{x}^{(2)} &= [-0.0834, 0.8820]^\top \\ \mathbf{f}(\mathbf{x}^{(2)}) &= [0.0800, 0.4152]^\top \\ \frac{\partial \mathbf{f}(\mathbf{x}^{(2)})}{\partial \mathbf{x}} &= \begin{bmatrix} 7.1160 & 2.7687 \\ -0.3510 & 7.4096 \end{bmatrix} \end{aligned}$$

$$\begin{aligned} \mathbf{x}^{(3)} &= [-0.0834, 0.8820]^\top \\ \mathbf{f}(\mathbf{x}^{(3)}) &= [0.0082, -0.0146]^\top \end{aligned}$$